



Lecture – 10

Combinational Array Multiplier

- Composed of arrays of simple combinational elements, each of which implements an add/sub and shift operation for small slices of the multiplicand operands.

- $X = x_{n-1}x_{n-2}\dots\dots x_1x_0$ and $Y = y_{n-1}y_{n-2}\dots\dots y_1y_0$ where both X and Y are unsigned integers. Now $P = X \times Y$ can be expressed as $P = \sum_{i=0}^{n-1} 2^i x_i Y$

which can be rewritten as
$$P = \sum_{i=0}^{n-1} 2^i \left(\sum_{j=0}^{n-1} x_i y_j 2^j \right)$$

- It requires $n \times n$ array of 2-input AND gate.
- The product terms are summed by an array of $n(n-1)$ 1-bit full adders.


Multiplication

$$\begin{array}{r}
 \text{X} \quad \begin{array}{r} 1000 \\ 1001 \\ \hline 1000 \\ 0000 \\ 0000 \\ 1000 \\ \hline 1001000 \end{array} \begin{array}{l} \text{Multiplicand } Y \\ \text{Multiplier } X = x_3x_2x_1x_0 \\ \text{Product} \end{array}
 \end{array}$$


$$P_{i+1} = P_i + x_j 2^i Y$$

- If multiplicand = ***n*** bits and multiplier = ***m*** bits then product = ***n + m*** bits.
- Two rules:
 - Place a copy of multiplicand in the proper place if multiplier bit=1.
 - Place 0 in the proper place if multiplier bit = 0.

Sequential Multiplication Algorithm

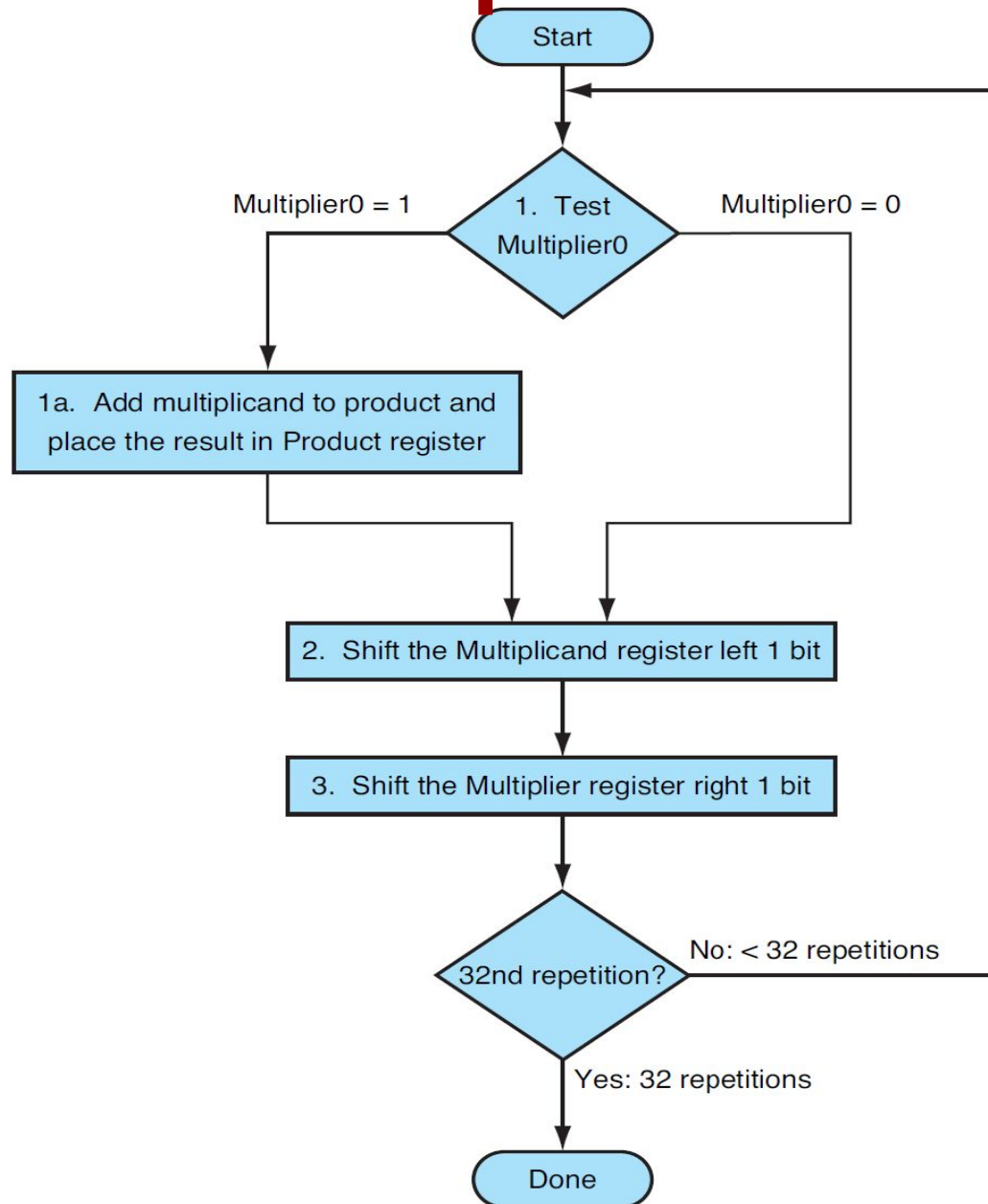


Sequential Multiplication Hardware

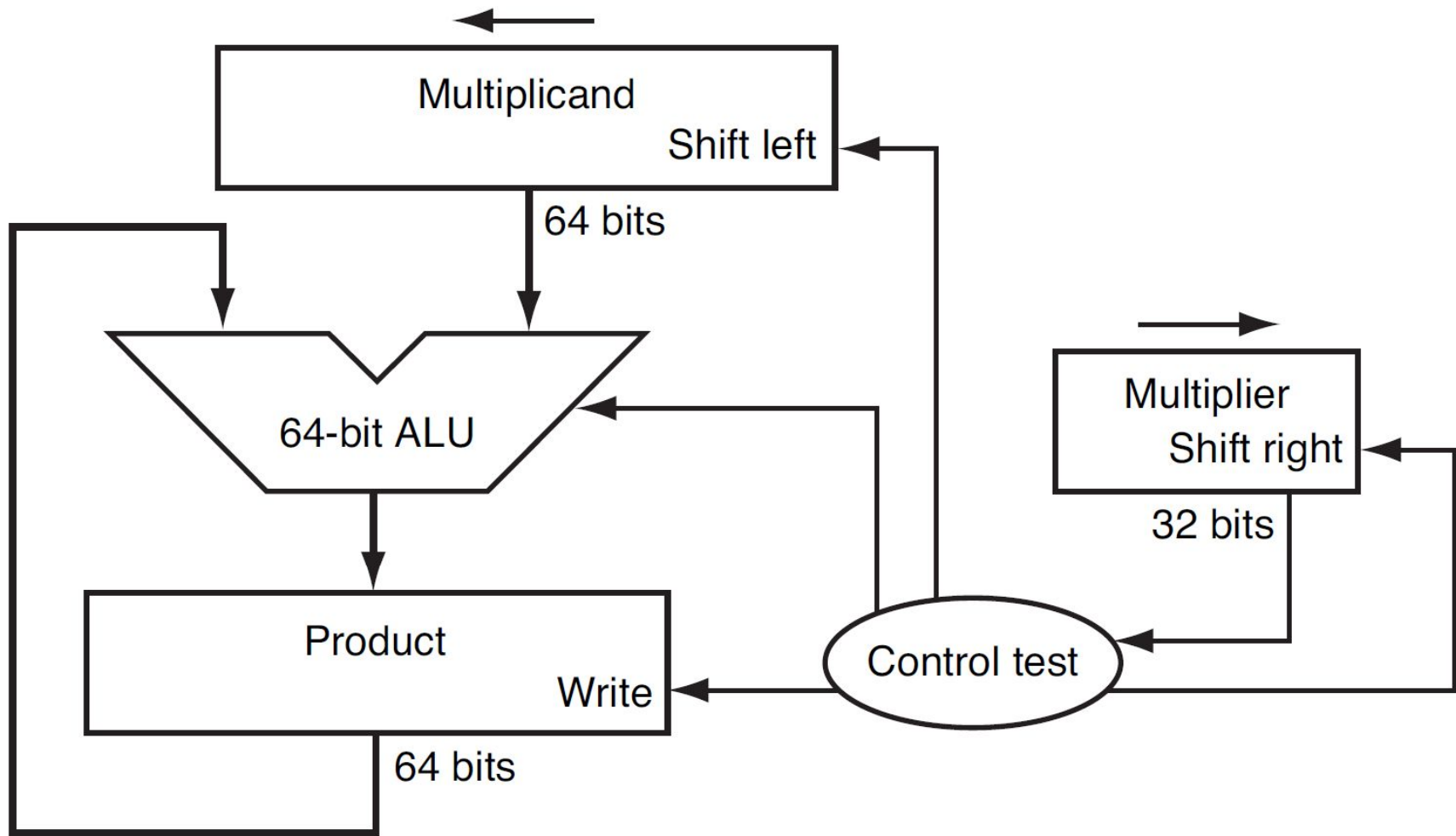


Sequential Multiplication Example

Iteration	Step	Multiplier	Multiplicand	Product
0	Initial values	001 ^①	0000 0010	0000 0000
1	1a: $1 \Rightarrow \text{Prod} = \text{Prod} + \text{Mcand}$	0011	0000 0010	0000 0010
	2: Shift left Multiplicand	0011	0000 0100	0000 0010
	3: Shift right Multiplier	000 ^①	0000 0100	0000 0010
2	1a: $1 \Rightarrow \text{Prod} = \text{Prod} + \text{Mcand}$	0001	0000 0100	0000 0110
	2: Shift left Multiplicand	0001	0000 1000	0000 0110
	3: Shift right Multiplier	000 ^②	0000 1000	0000 0110
3	1: $0 \Rightarrow$ No operation	0000	0000 1000	0000 0110
	2: Shift left Multiplicand	0000	0001 0000	0000 0110
	3: Shift right Multiplier	000 ^③	0001 0000	0000 0110
4	1: $0 \Rightarrow$ No operation	0000	0001 0000	0000 0110
	2: Shift left Multiplicand	0000	0010 0000	0000 0110
	3: Shift right Multiplier	0000	0010 0000	0000 0110

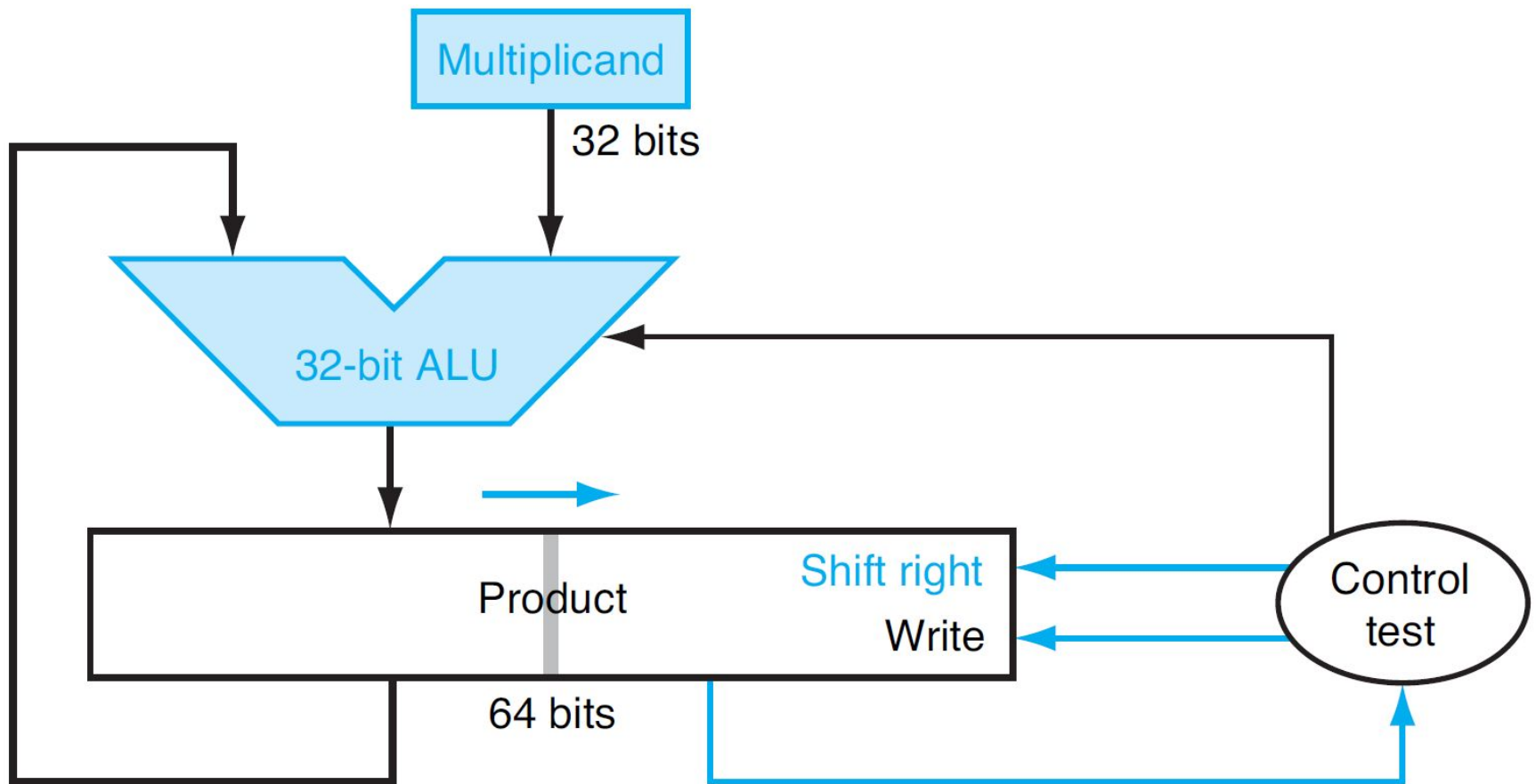
Refined Version of Multiplication Hardware



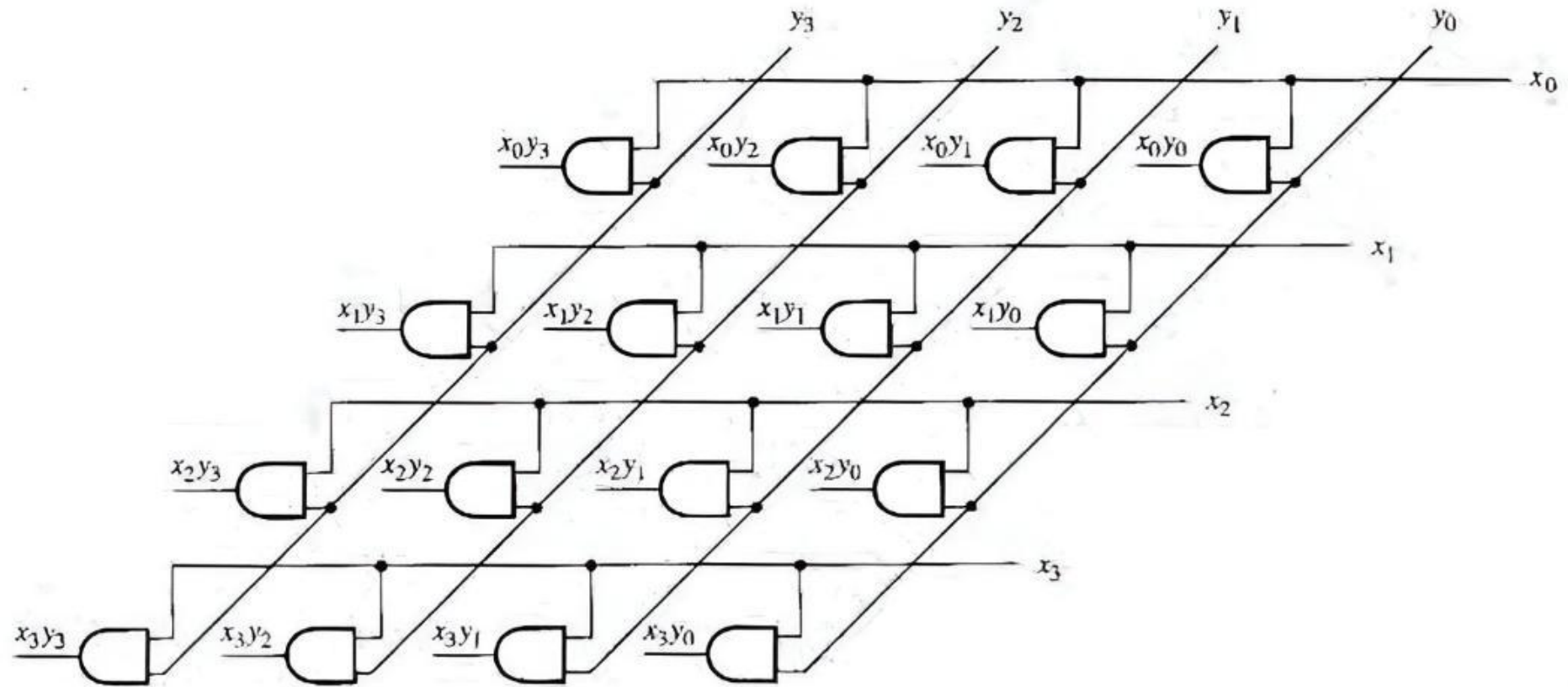AND Array for 4 X 4 bit Unsigned Multiplication



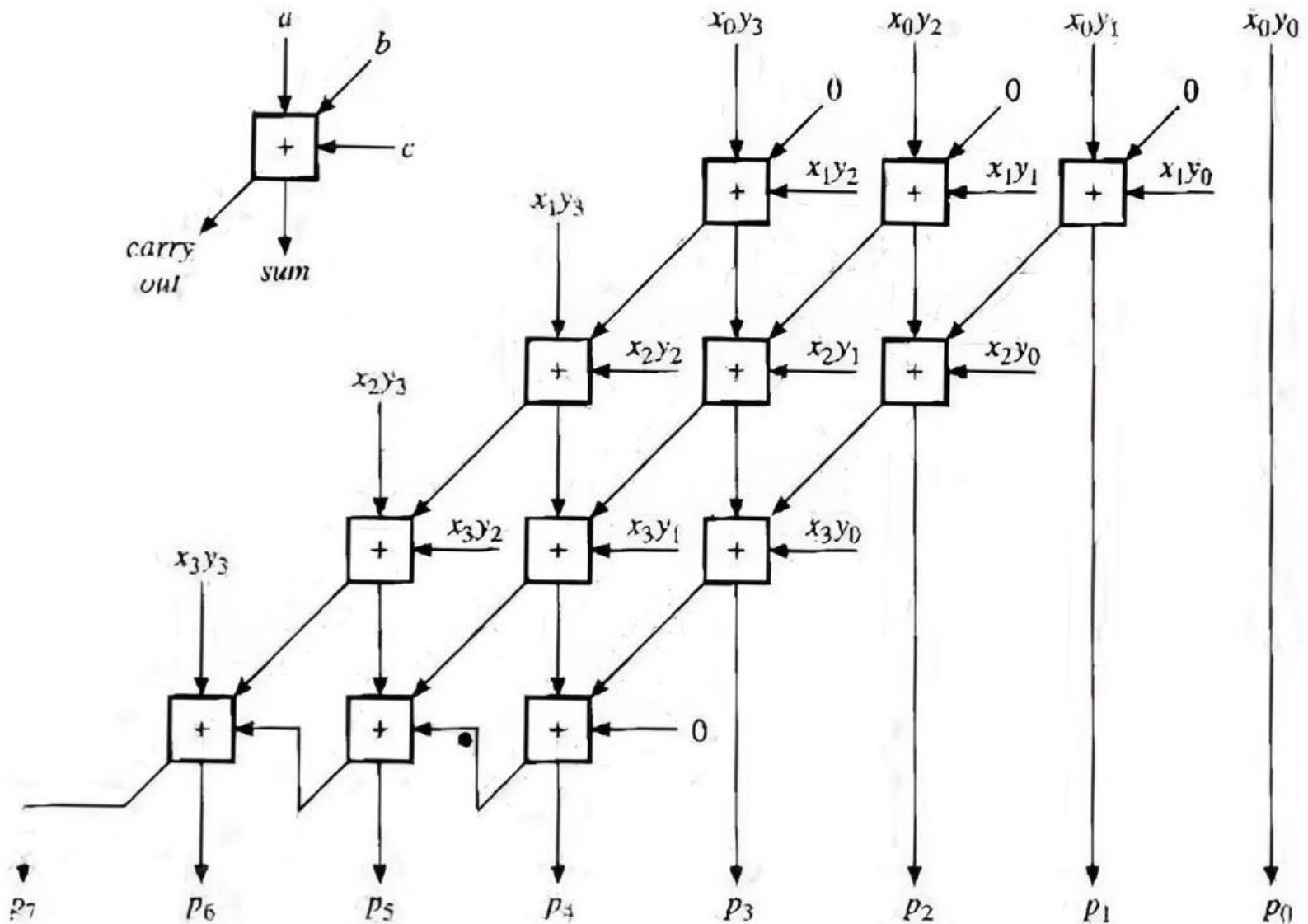
Full Adder Array for 4 X 4 bit Unsigned Multiplication




Division

	1001_{ten}	Quotient
Divisor 1000_{ten}	$\overline{)1001010_{\text{ten}}}$	Dividend
	$\underline{-1000}$	
	10	
	101	
	1010	
	$\underline{-1000}$	
	10_{ten}	Remainder

Division Hardware

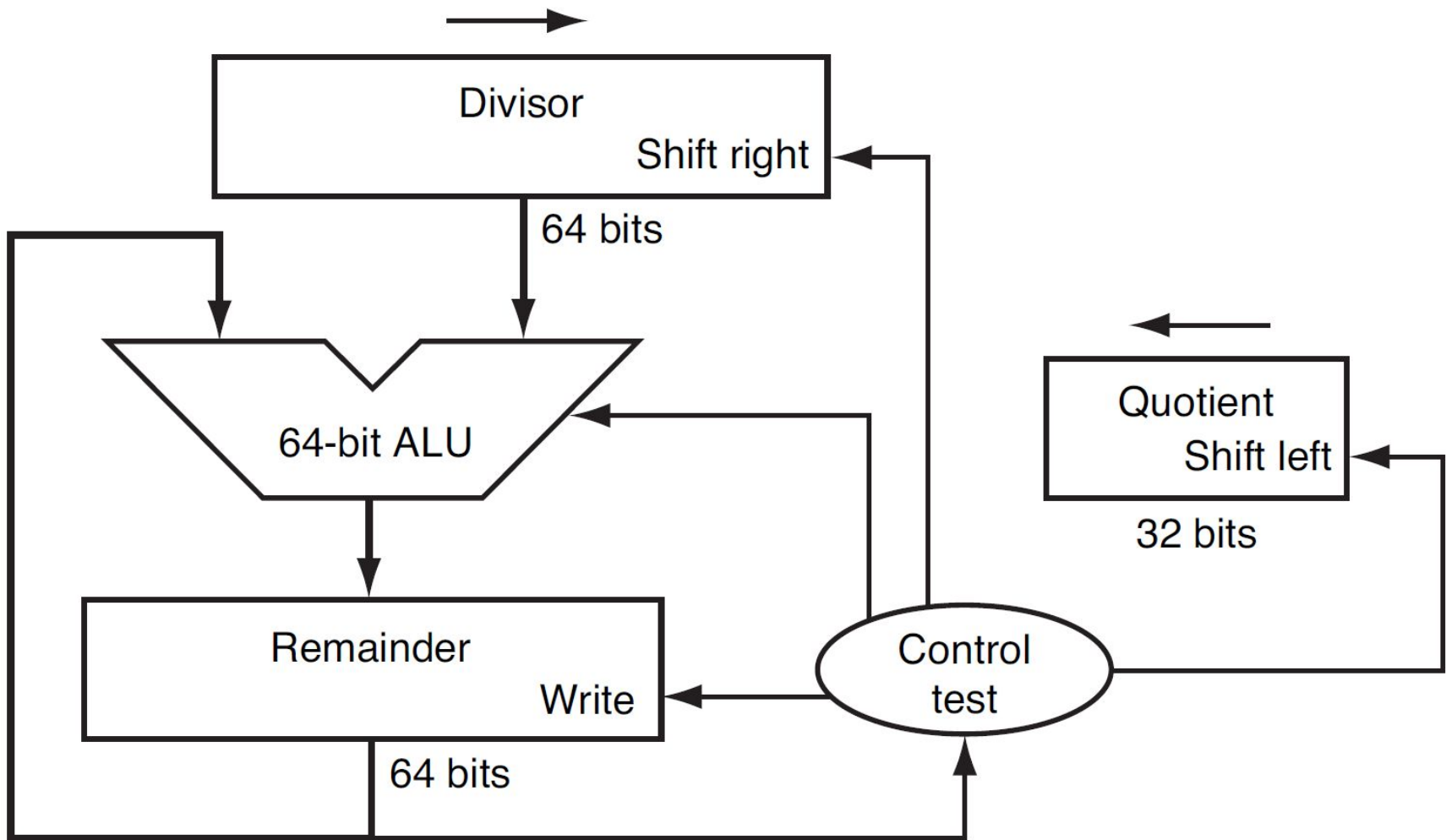

Division Algorithm

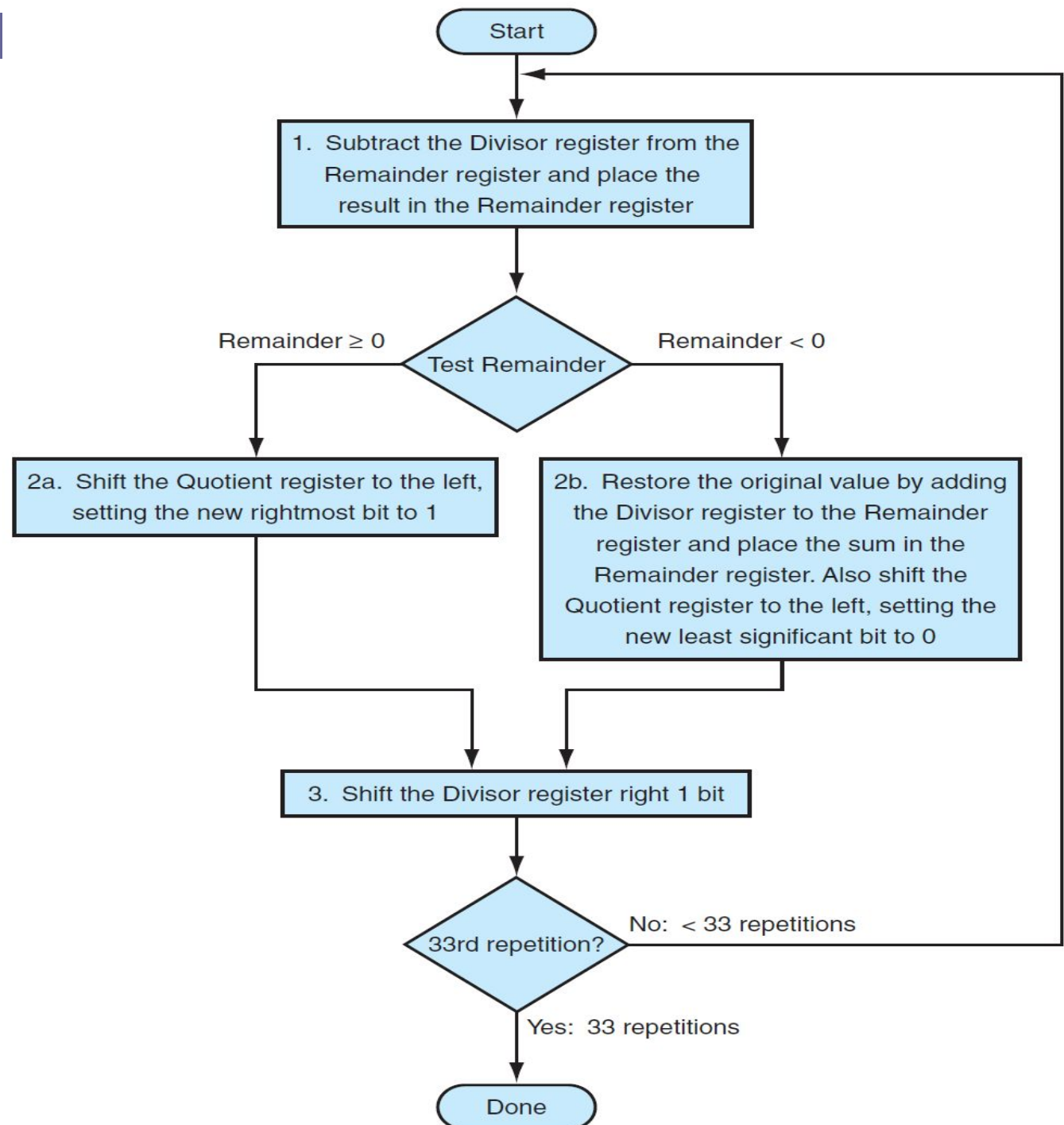

Division Example

Iteration	Step	Quotient	Divisor	Remainder
0	Initial values	0000	0010 0000	0000 0111
1	1: Rem = Rem – Div	0000	0010 0000	①110 0111
	2b: Rem < 0 \Rightarrow +Div, sll Q, Q0 = 0	0000	0010 0000	0000 0111
	3: Shift Div right	0000	0001 0000	0000 0111
2	1: Rem = Rem – Div	0000	0001 0000	①111 0111
	2b: Rem < 0 \Rightarrow +Div, sll Q, Q0 = 0	0000	0001 0000	0000 0111
	3: Shift Div right	0000	0000 1000	0000 0111
3	1: Rem = Rem – Div	0000	0000 1000	①111 1111
	2b: Rem < 0 \Rightarrow +Div, sll Q, Q0 = 0	0000	0000 1000	0000 0111
	3: Shift Div right	0000	0000 0100	0000 0111
4	1: Rem = Rem – Div	0000	0000 0100	①000 0011
	2a: Rem \geq 0 \Rightarrow sll Q, Q0 = 1	0001	0000 0100	0000 0011
	3: Shift Div right	0001	0000 0010	0000 0011
5	1: Rem = Rem – Div	0001	0000 0010	①000 0001
	2a: Rem \geq 0 \Rightarrow sll Q, Q0 = 1	0011	0000 0010	0000 0001
	3: Shift Div right	0011	0000 0001	0000 0001